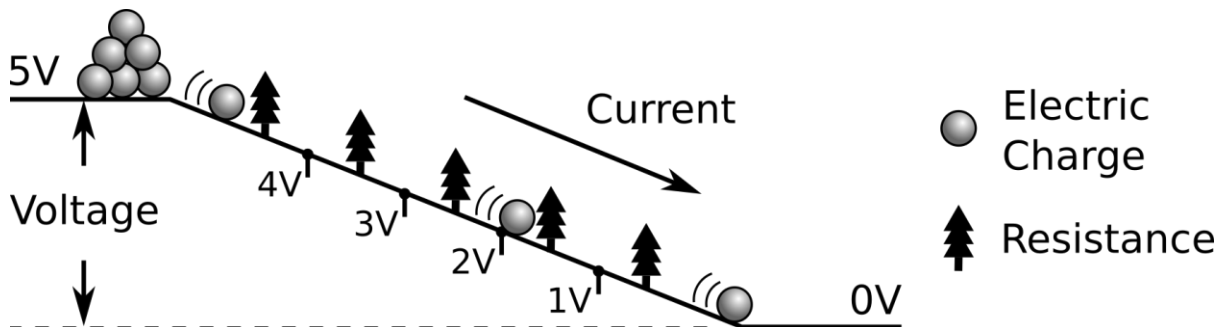


# HIMALAYAN MAKERS GUILD


## Foundation Activity 11

### Voltage Divider Nightlight

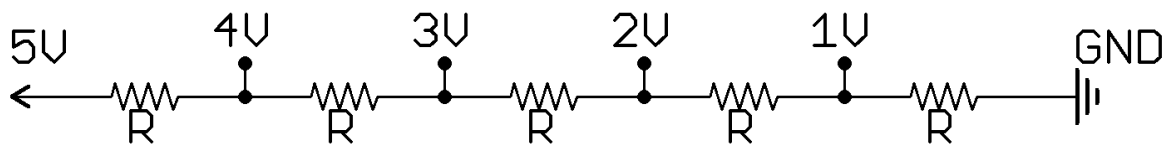
#### VOLTAGE DIVIDER




As **current** (moving electric charge) flows through a **resistance** (trees), **voltage** (height of the hill) is dropped. All of the voltage must be dropped across the resistors. As a circuit diagram, it looks like this:



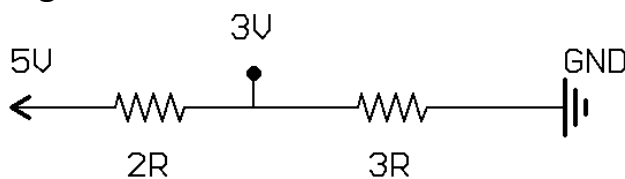
If all the resistors are the same, an equal amount of voltage is dropped across each one (1 V per resistor). The amount of voltage dropped across a resistor depends on how big its resistance is compared to the total resistance between 5V and 0V. Since the voltage is divided across the resistors, we call this a **voltage divider**.



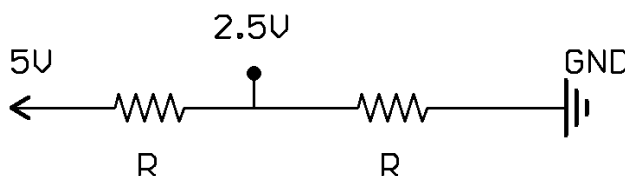If we have one resistance of  $2R$ , and another of  $3R$ , more voltage will be dropped across the  $3R$  resistor.



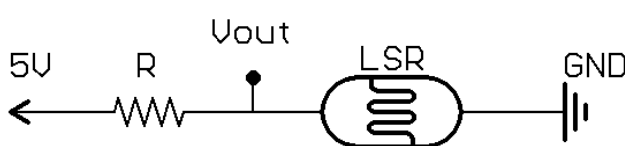If we have two equal resistances, the voltage will be dropped equally across both of them (2.5V).




A Light Dependent Resistor (**LDR**) changes resistance depending the amount of light shining on it. **Vout** will change depending on the amount of light.
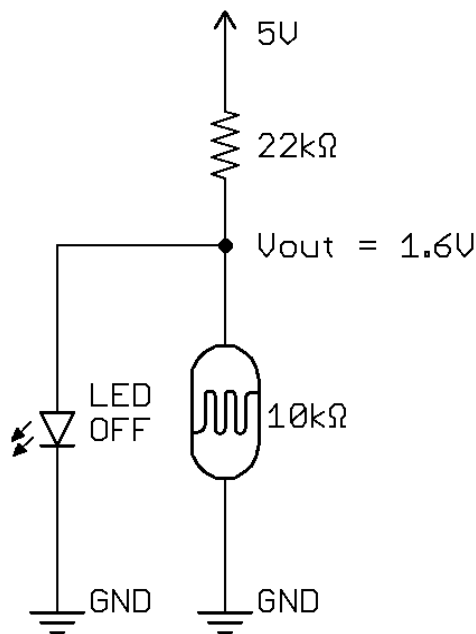
## BUILDING A NIGHTLIGHT CIRCUIT


We can use an **LDR** in a voltage divider to make a night-light. If **V<sub>out</sub>** is greater than 3 V the LED will be **ON**. If V<sub>out</sub> is less than 3V, the LED turns **OFF**.

In this voltage divider, we have chosen R to have a resistance of 22 k $\Omega$  (22000  $\Omega$ ). The other resistor (220  $\Omega$ ) is usually used protect the LED from high current when powering it from 5V.



When there is light, the LDR has a small resistance.

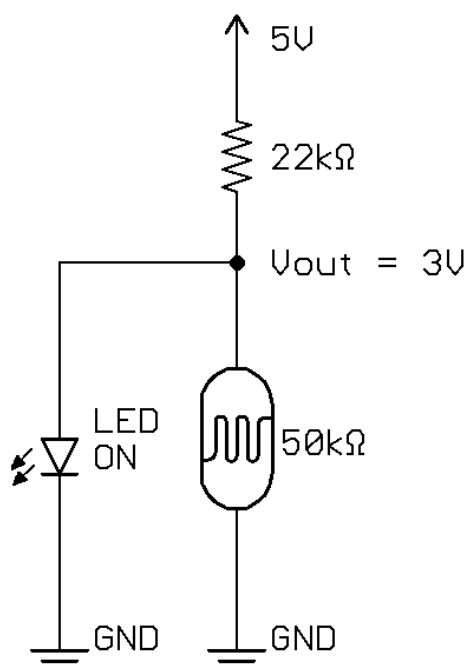The LDR becomes much **less than** 22k $\Omega$ , so V<sub>out</sub> drops **below** 3V and the LED turns **OFF**.



When it is dark, the LDR has a big resistance.

The LDR much **greater than** 22k $\Omega$ , so V<sub>out</sub> rises **above** 3V and the LED turns **ON**.

How does the brightness of the LED compare to when we power it directly with 5V through the 220 $\Omega$  resistor? What could be causing this difference?

<sup>1</sup> Sun and moon icons made by Freepik from [www.flaticon.com](http://www.flaticon.com)